



March 2007 Meeting

S.K. Wood

1. Introduction




- A summary of the work carried out on mapping repetitive structures to VHDL.
 - What has happened - Following on from the last meeting:
 - Creating VHDL examples and generic templates
 - What is happening
 - Work on non-trivial examples for publication
 - What to do next
- ?

 2. Past work




- ArrayOL to represent repetitive component structures –
- VHDL implementations carried out to identify required transformations:

- X and Y-plane repetition of basic elementary tasks.



 - The perfect shuffle algorithm.
- X-plane repetitions of the perfect shuffle.





• Perfect shuffle

```
1.  entity shuffle_A is
2.  generic (Origin: Integer:= 0;ArraySize: Positive:= 8; P_Lim: Positive:= 4; F_Lim: Positive:= 2);
3.  Port(
4.      A_IN: in std_logic_vector (0 to ArraySize -1);
5.      A_OUT: out std_logic_vector(0 to ArraySize -1)
6.  );
7.  end shuffle_A;

9.  architecture Behav of shuffle_A is
10.     signal reshape: std_logic_vector (0 to ArraySize -1); -- interconnects
11.     component B
12.         Port(
13.             B_IN: in std_logic_vector(0 to 2-1);
14.             B_OUT: out std_logic_vector(0 to 2-1)
15.         );
16.     end component;
17.     begin
18.         TILERS:for i in Origin to Origin + P_Lim -1 generate
19.             Source:B port map (B_IN(0)=> A_IN (i*F_Lim),B_IN(1)=> A_IN (i*F_Lim+1),B_OUT(0)=>reshape(i*F_Lim),B_OUT(1)=>reshape(i*F_Lim+1));
20.             Target:B port map (B_IN(0)=>reshape(i),B_IN(1)=>reshape(i+P_Lim),B_OUT(0)=> A_OUT (i*F_Lim),B_OUT(1)=> A_OUT (i*F_Lim+1));
21.         end generate TILERS;
22.     end Behav;
```



• Simplified Tilers for Shuffle

17. TILERS:for i in 0 to 4 -1 generate

18. Source:B port map (

B_IN(0)=> A_IN (i*2),

B_IN(1)=> A_IN(i*2+1),

B_OUT(0)=>rehape(i*2),

B_OUT(1)=>rehape(i*2+1));

19. Target:B port map (



B_IN(0)=>rehape(i),

B_IN(1)=>rehape(i+4),

B_OUT(0)=> A_OUT (i*2),

B_OUT(1)=> A_OUT (i*2+1));


20. end generate TILERS;

 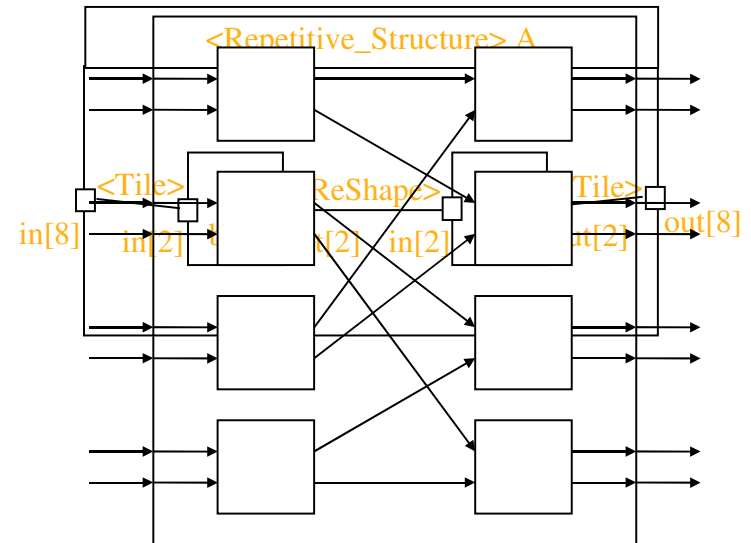



• Simplified Tilers for Shuffle



- When index $i = 0$

 

$B_OUT(0) \Rightarrow \text{rehape}(i*2), = 0$ $B_IN(0) \Rightarrow \text{rehape}(i), = 0$
 $B_OUT(1) \Rightarrow \text{rehape}(i*2+1), = 1$ $B_IN(1) \Rightarrow \text{rehape}(i+4), = 4$



 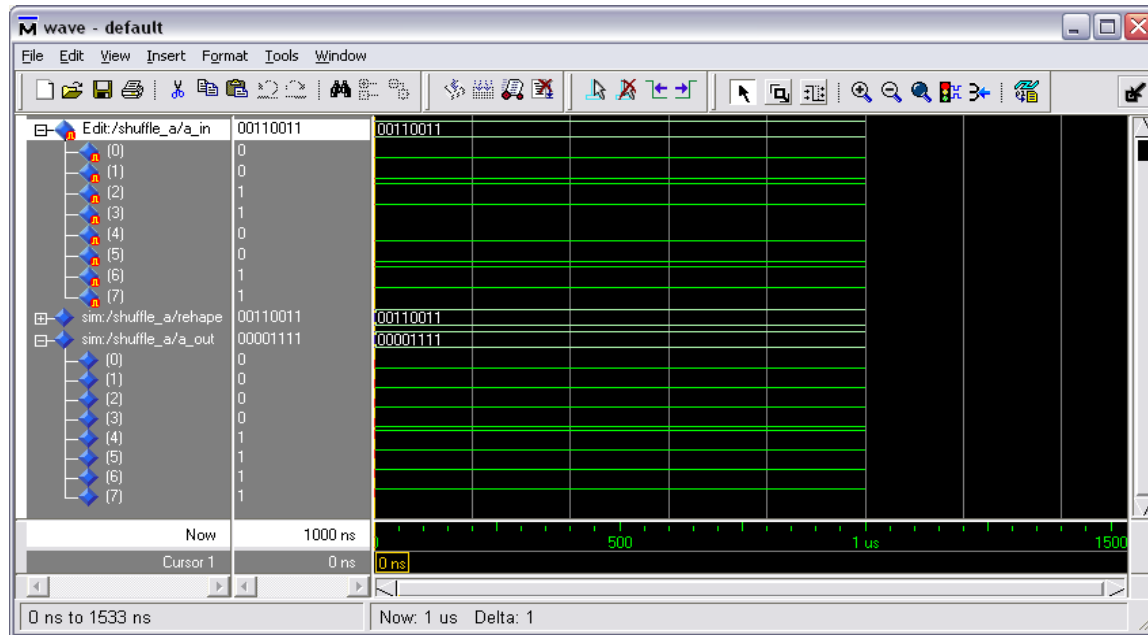- Test-bed simulations of these examples
 - To verify their operation against a set of conventionally coded port-map examples.





- The examples considered so far are considered as minor manipulations of structures comprised of basic elementary components; and as such, not of significant scientific interest to the world of embedded system design.
- Such examples are generated with minimal effort by VHDL software engineers.
- The benefit of alternative method of describing them is not apparent.



- A non-trivial example is required to demonstrate the use of the ArrayOL extension in the modelling tool to describe repetitive component structures.
- Need to present the case of an example that is significant in the design of embedded systems.




4. Current Work

- In search of a more challenging example: I have considered a CORDIC pipeline processing stage, as used in implementations of Fast Fourier Transforms.
- CORDIC is an acronym for **CO**ordinate **R**otation **D**igital **C**omputer, which forms part of a class of shift-add algorithms for rotating vectors in a plane.
- Vector rotation is useful in a host of DSP applications including modulation and Fourier Transforms.



The CORDIC pipeline structure

 - The COORDIC processor stage can be described as an array of interconnected 'adder-subtractor' stages.




- Thus, this component repetition in the X-Plane is ideally suited for an ArrayOL description.



The elementary components

- A single 'Adder-Subtractor' stage

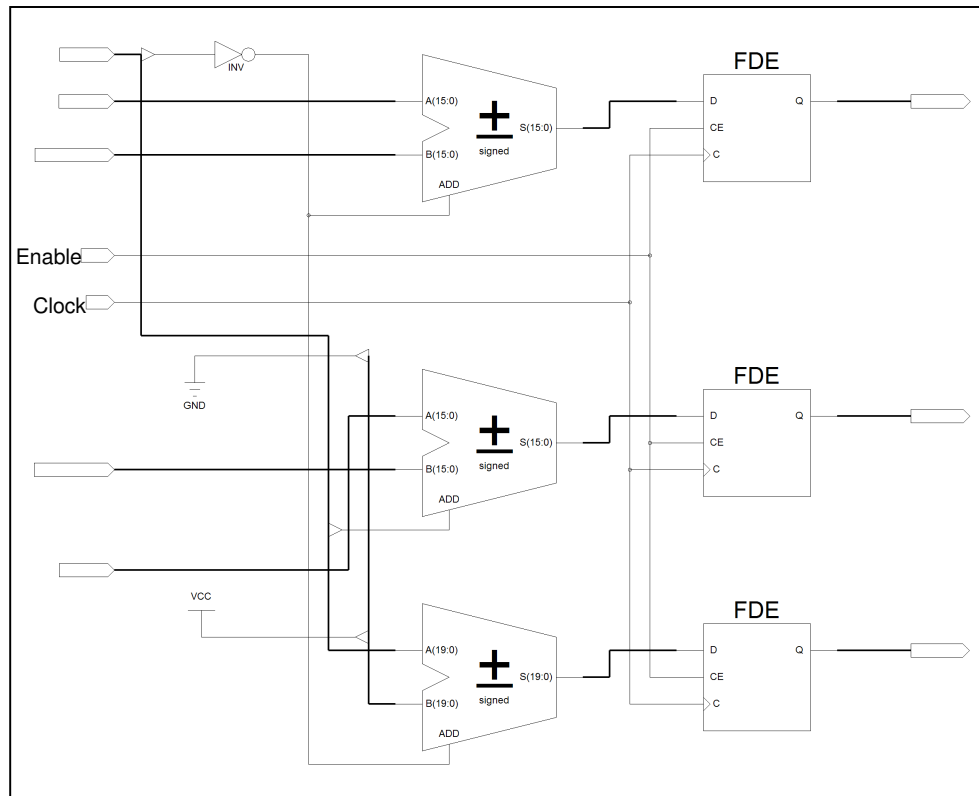


Not really concerned with the function of this stage at this time.

Description of the elementary components (*continued*)



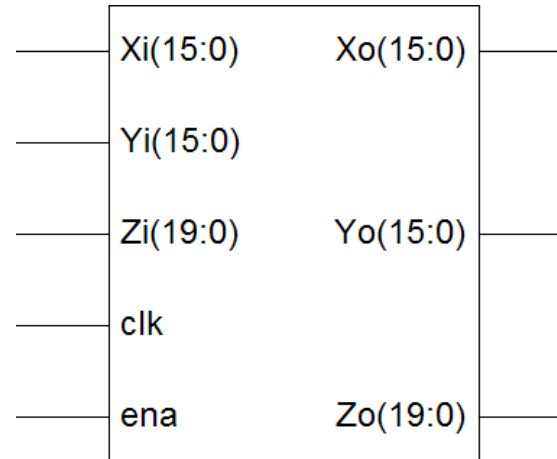- Component entity description of the 'Adder-Subtractor' stage



- We can consider the stage as a 'black box' with identified ports.



- **BUT . . .**
- When the 'Adder-Subtractor' stage is considered as an elementary component in this way. . .
- This example degenerates into little more than those previously considered ☹️
- The complexity of this example lies not with the repetition of components, but with the architecture of the component entities.



- ~~Have I been wasting my time ?~~
- The real question is . . .
 - Is it in fact that repetitive structures are themselves trivial and as such require only trivial examples ??



5. Future work

- Having identified how ArrayOL can be used to describe the VHDL port map constructs
 - And what attributes need to be handled . . .
- The next stage would be to write the necessary transformation rules.
- To replicate a component, we first need to be able to model it as an entity with definable ports.
 - This is an issue which came apparent when attempting to integrate state machines into other architectures, and is currently being addressed.



- That concludes my section of this mornings presentations

Thank You